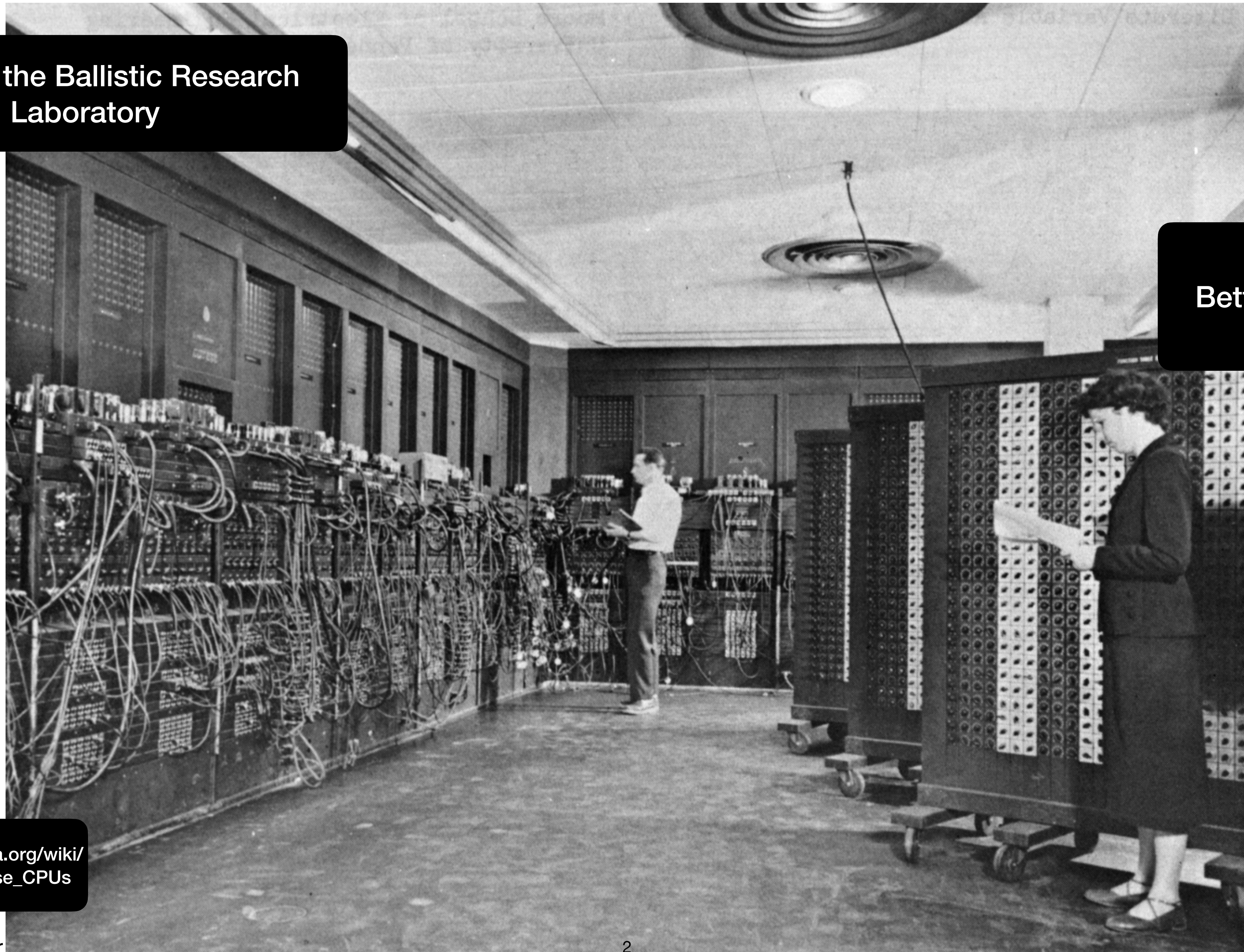


Building a Basic Processor: The Components

ENIAC at the Ballistic Research Laboratory


Betty Snyder



Source: https://en.wikipedia.org/wiki/History_of_general-purpose_CPUs


From Wednesday... Multiplexers

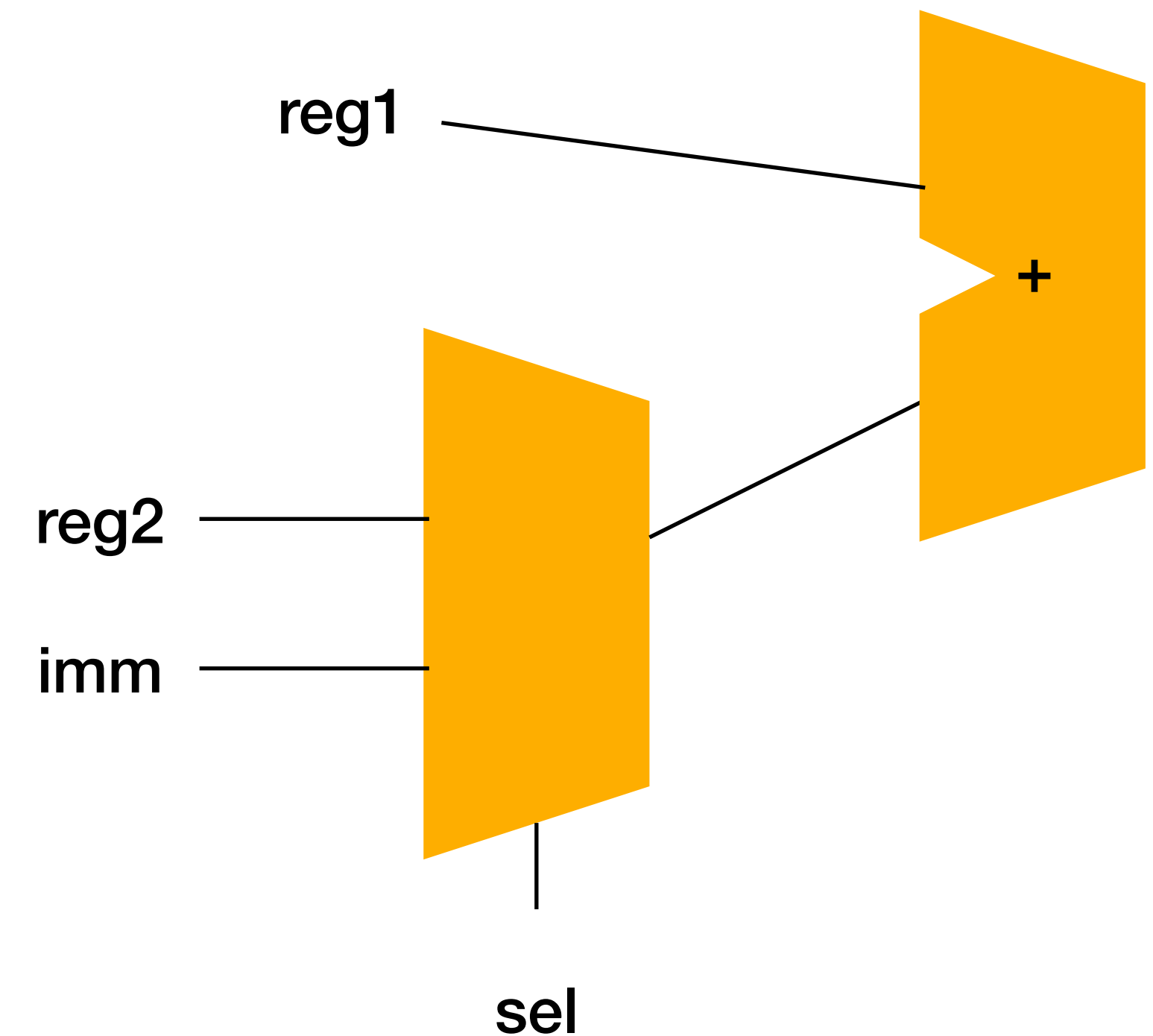- “Hardware if-statements”
- Select between multiple inputs
- Example: choose the second operand for add and addi




Chat with your neighbor(s)!

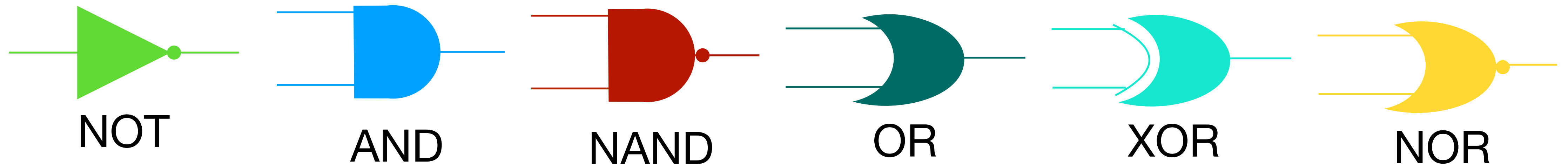Build a two-input (1-bit selector) MUX out of logic gates!



Build a Two-Input (1-bit selector) MUX!

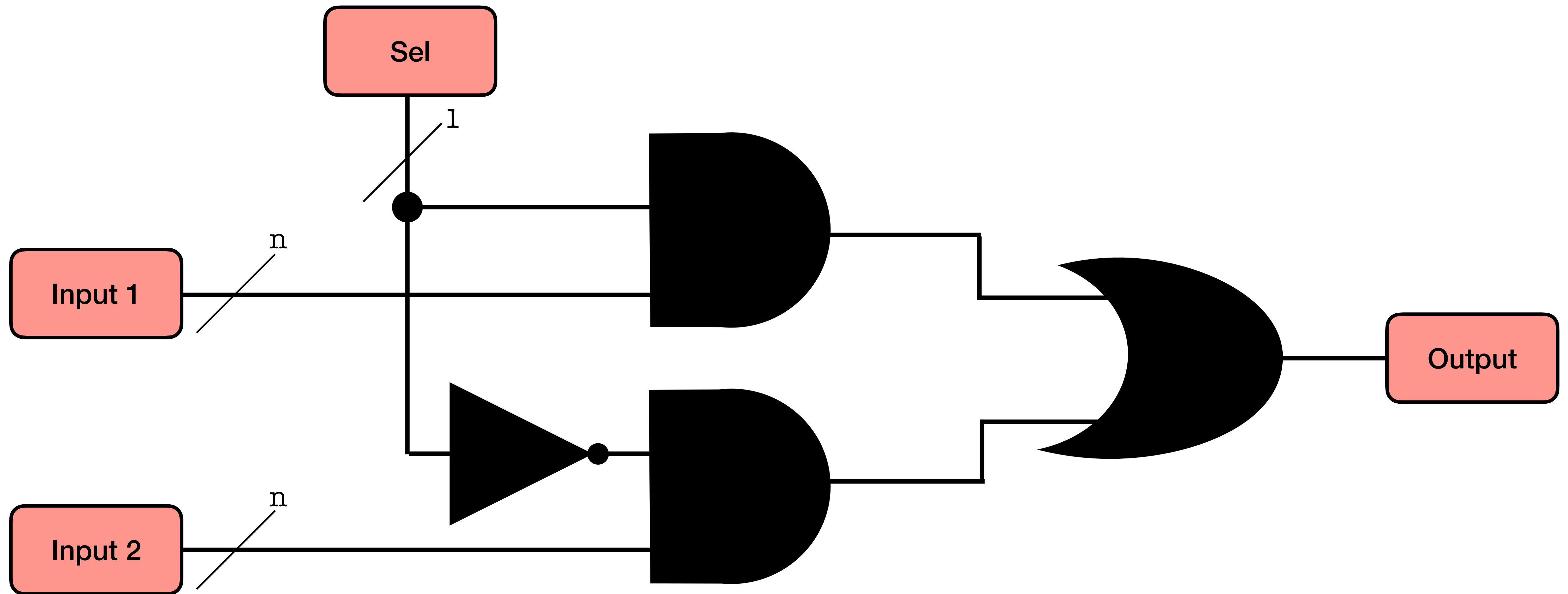


Outline

- Reintroducing the goals of a processor
- Overview of data path elements
- Constructing a data path

Processor Goals

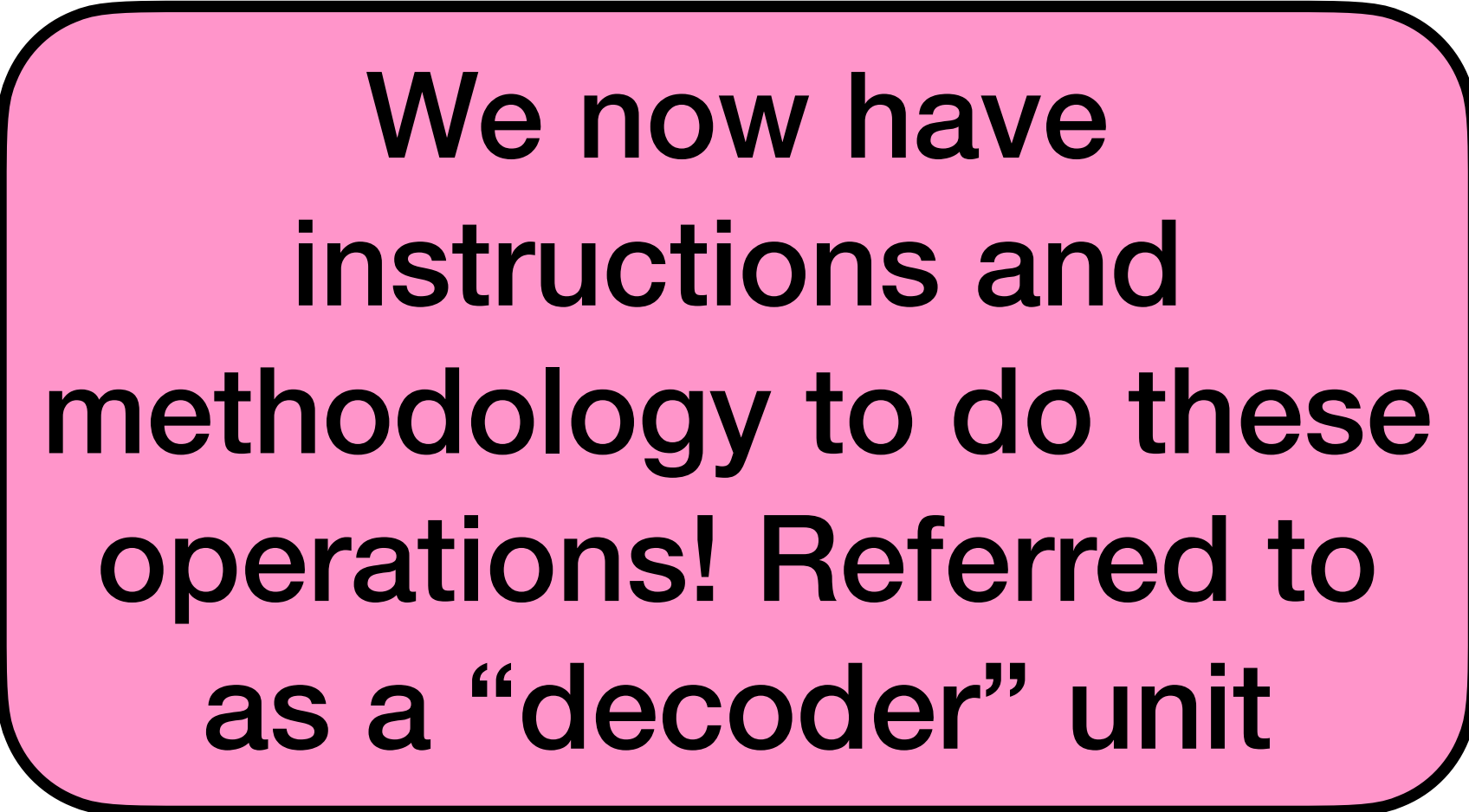- Track the location of what to execute
- Fetch instructions from memory
- Interpret instructions
- Execute instructions
- Maintain and update state




**We now have
instructions and
methodology to do these
operations! Referred to
as a “decoder” unit**

Program Counter (PC)


- After each instruction, we need to know what to fetch next
- The *program counter* is a special purpose register (maintains state) to tell the processor which instruction to fetch next
- How does the processor know what the next PC state should be?
- Demo!

Instruction Memory

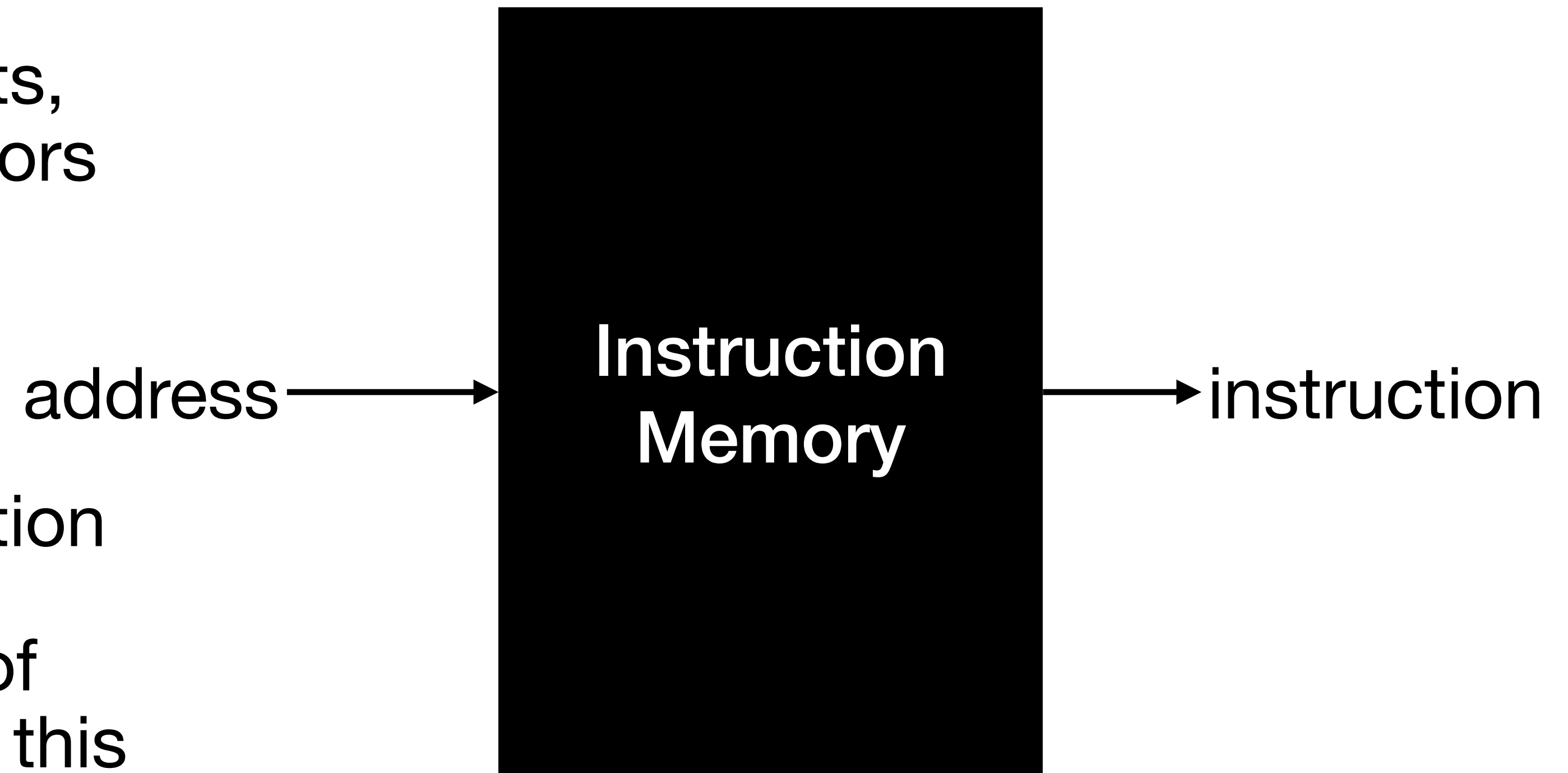- Just like combinational logic units, memory is composed of transistors (and capacitors)!
- Takes address as input
- Returns raw bytes of the instruction
- Over simplification for the sake of basic processor! We will explore this in more detail next module



Processor Goals: Fetching Instructions

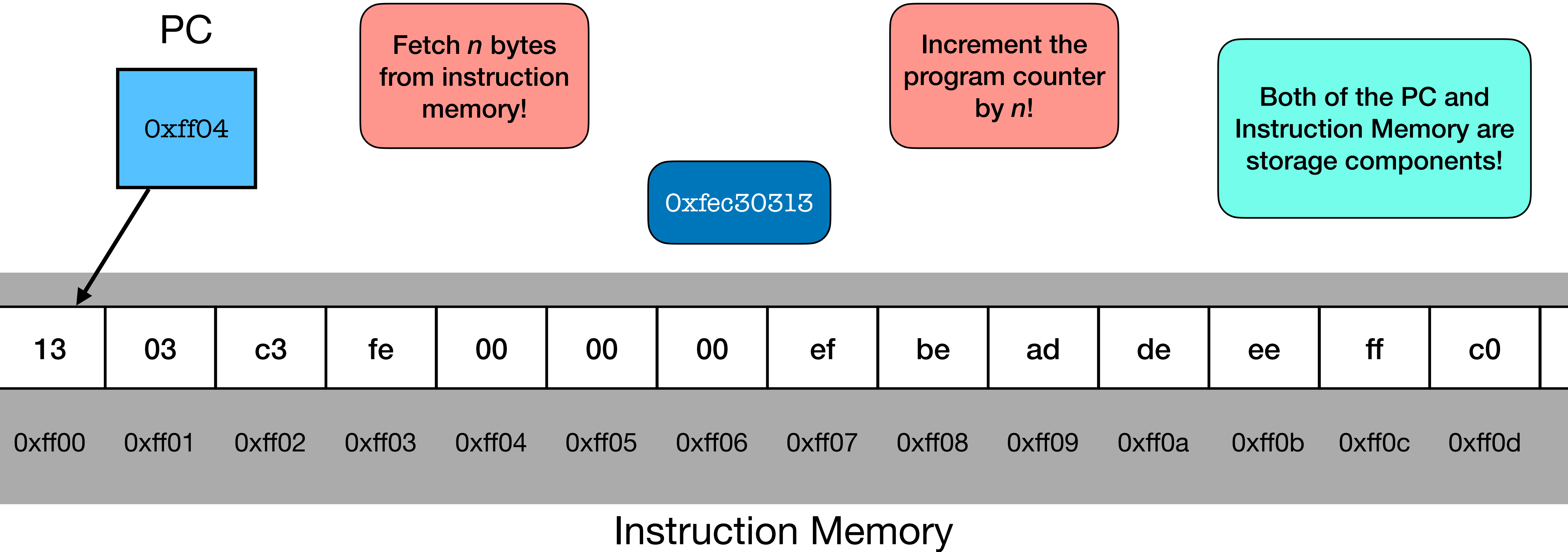

Processor Goals: Execute Instructions

- What components do we need to execute instructions? Remember how our instructions can be defined!
- Instructions refer to register/memory locations where data should be stored
- Instructions refer to some functionality to manipulate data




Data Transfers

Computations

Control Logic

Register File

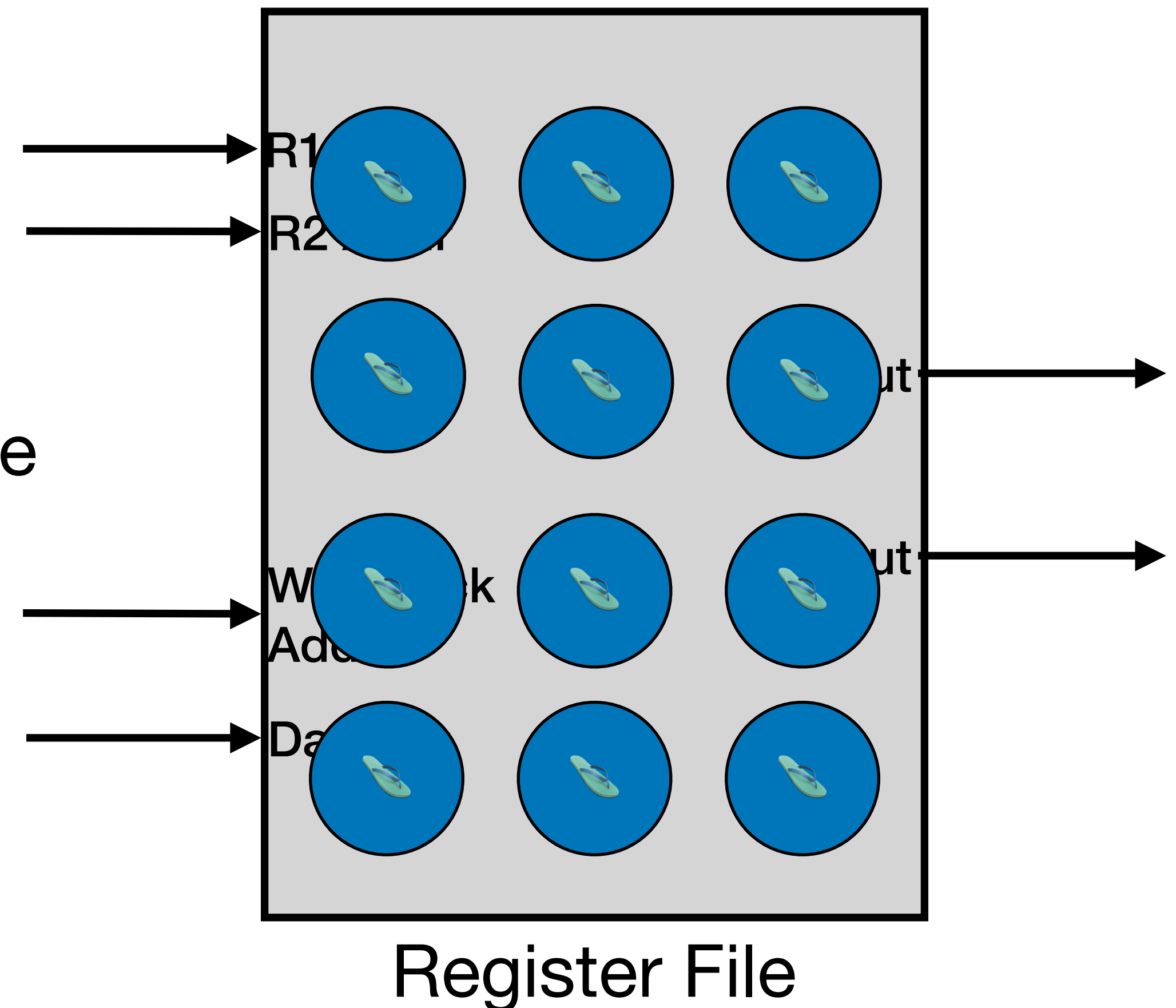- Takes in four inputs: register addresses to “get” (R1 and R2), any data to write, and the destination it should be written to
- Registers composed of flip flops to store the data
- Reading state happens on the “rising edge” of the clock cycle whereas updates to state happen on the “falling edge” of the clock cycle




Chat with your neighbor(s)!

Suppose a processor is executing the instruction `add x1, x1, x1`. How will this be interpreted by the register file?


Computational Units

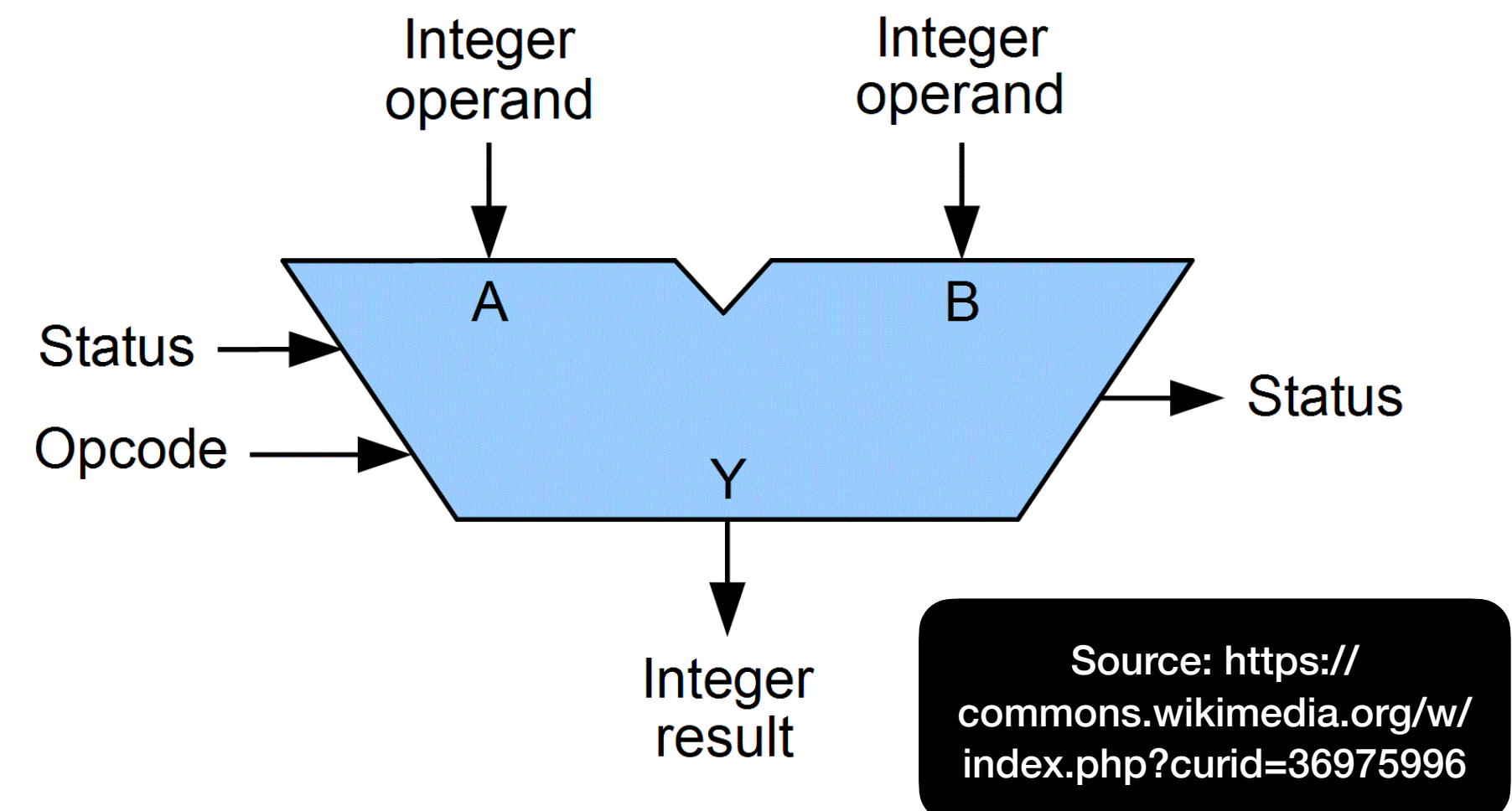- Arithmetic Logic Unit (ALU): a large combinational logic unit for arithmetic operations
- Integer operands (inputs) passed to the ALU with values to operate on
- Takes “opcode” as input to determine which functionality to use where functionality is implemented as a “pure function” from combinational logic
- Produces integer result; status output used to detect overflows, exceptions, etc.




Data Memory

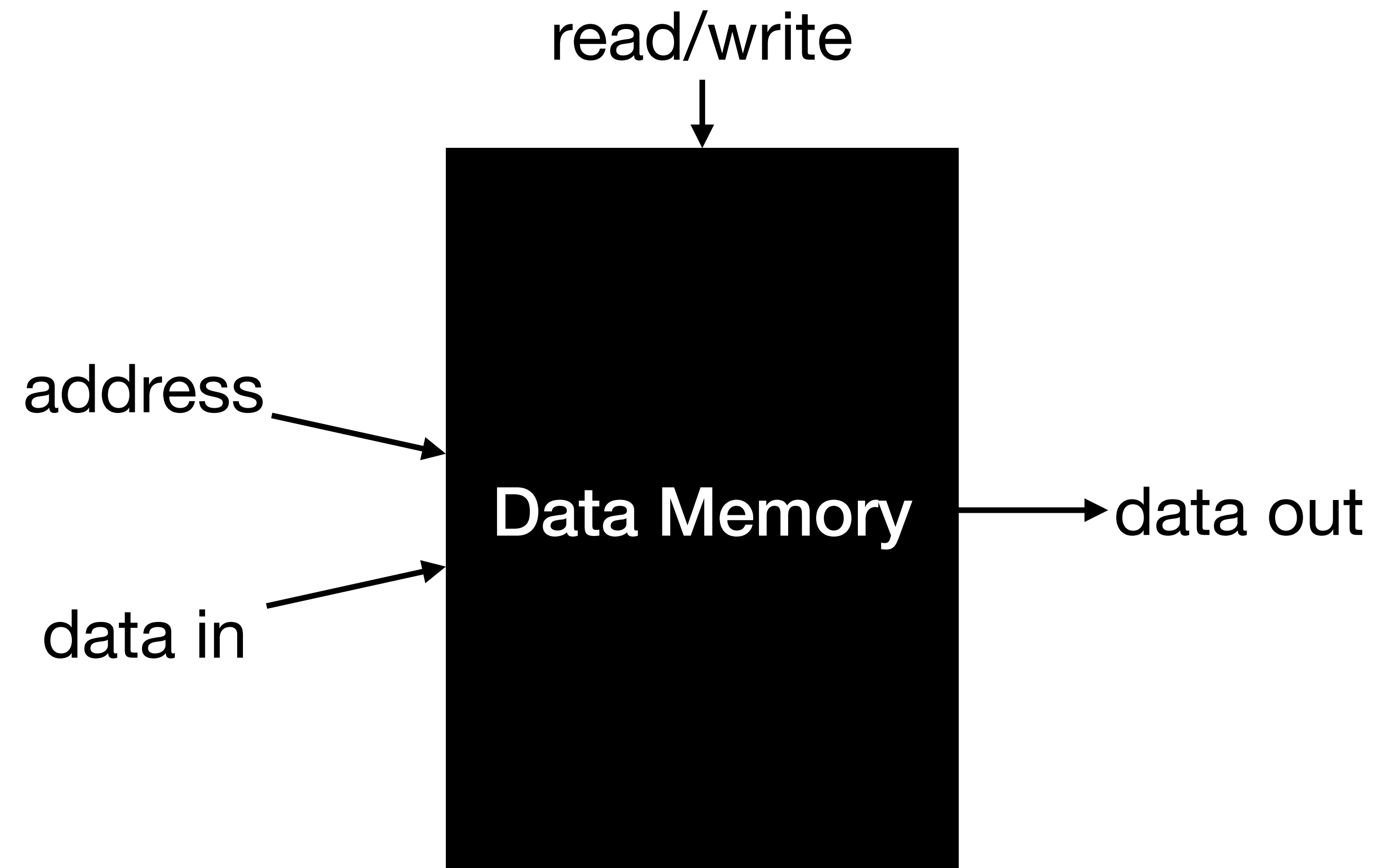- Much like instruction memory, data memory is composed of transistors/capacitors
- Data may be read or written, so there is an additional control signal that this component uses as input
- Data out only set if input signal is set to read
- Data in only used if input signal is set to write



Takeaways

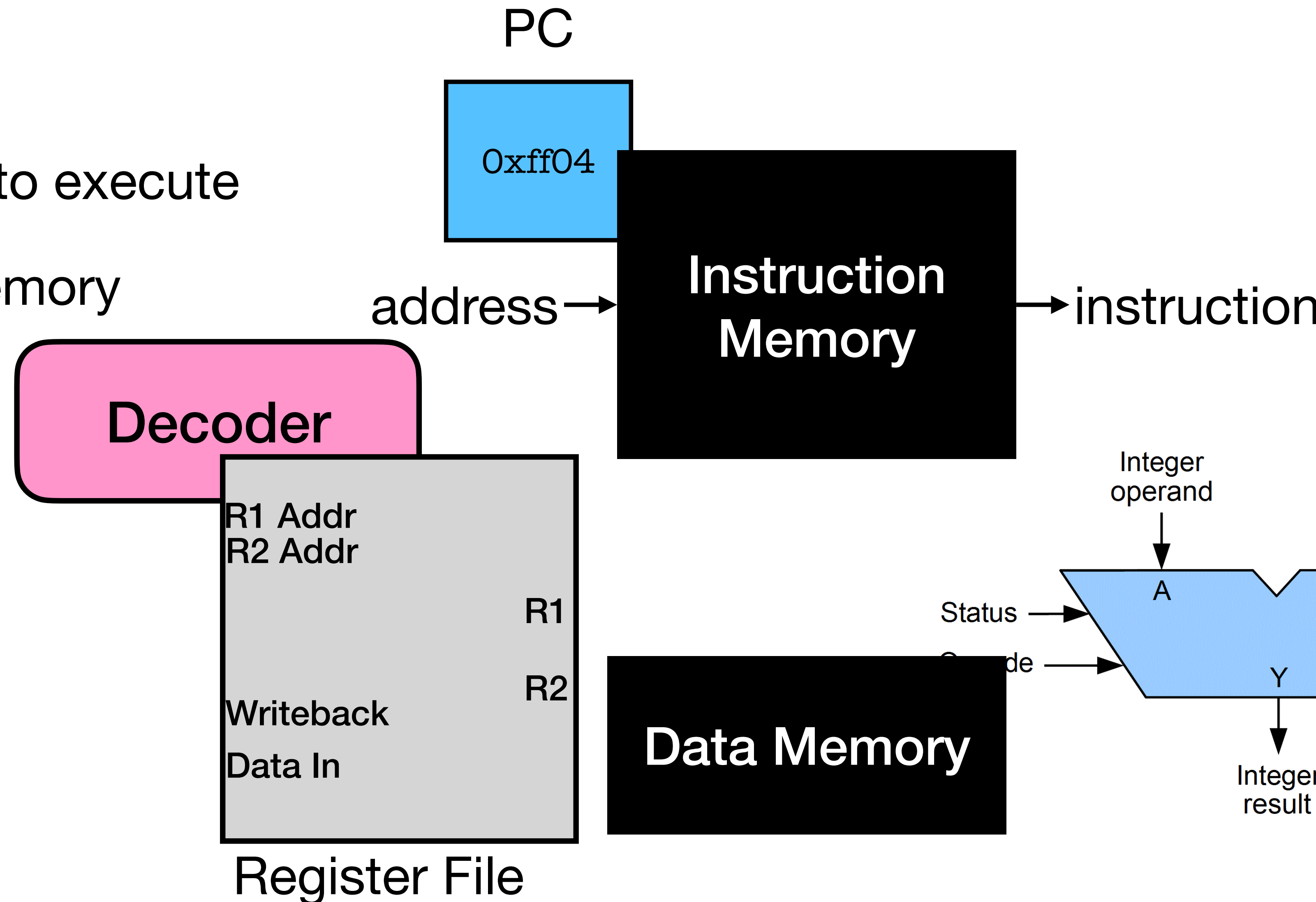- Track the location of what to execute
- Fetch instructions from memory
- Interpret instructions
- Execute instructions
- Maintain and update state



Exit Ticket!



<https://forms.cloud.microsoft/r/jZpZnu9Mas>