

DIGITAL CIRCUITS

David Kauchak
CS52 – Fall 2015

Admin

Assignment 4 due Monday at 11:59pm

Assignment 5 posted soon

- due Friday Oct. 23rd, at 5pm

CS lunch today!

Midterm

Average: 23.25

Top quartile: 26


Top half (median): 24.6

Bottom quartile: 21.4


Diving into your computer



Normal computer user

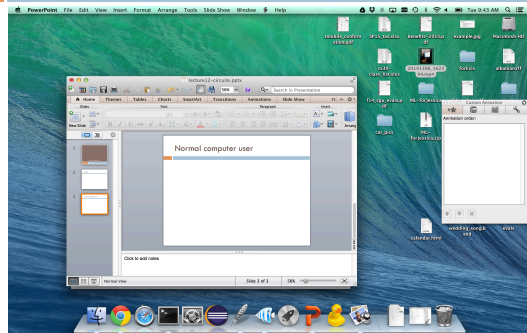

After intro CS

 

```

1 import objectDraw.*
2
3 public class Frog {
4     // Height of the frog image
5     private static final double FROG_HEIGHT = 48;
6
7     // This should refer to the image of the frog. Note that it is not
8     // the code we have provided.
9     private VisibleImage frogImage;
10
11     public Frog() {
12
13     }
14
15
16     public boolean overlaps(VisibleImage vehicleImage) {
17         return false; // YOU NEED TO CHANGE THIS!
18     }
19
20     public void kill() {
21
22     }
23
24     public void reincarnate() {
25
26     }
27
28     public void hopToward(Location point) {
29
30     }
31
32
33     public boolean isAlive() {
34         return false; // YOU NEED TO CHANGE THIS!
35     }
36
37 }
    
```

After 5 weeks of cs52

```

1 import objectDraw.*
2
3 public class Frog {
4     // Height of the frog image
5     private static final double FROG_HEIGHT = 48;
6
7     // This should refer to the image of the frog. Note that it is not
8     // the code we have provided.
9     private VisibleImage frogImage;
10
11     public Frog() {
12
13     }
14
15
16     public boolean overlaps(VisibleImage vehicleImage) {
17         return false; // YOU NEED TO CHANGE THIS!
18     }
19
20     public void kill() {
21
22     }
23
24     public void reincarnate() {
25
26     }
27
28     public void hopToward(Location point) {
29
30     }
31
32
33     public boolean isAlive() {
34         return false; // YOU NEED TO CHANGE THIS!
35     }
36
37 }
    
```



```

101 r1 r0 0      ; get a value for a
102 r2 r0 0      ; get a value for b
103 r3 r0 0      ; result = 0;
104
105
106 bte r1 r0 endloop ; test if a <= 0
107
108 add r3 r3 r2   ; result += b;
109 sbc r1 r1 1    ; a--;
110 btl r1 loop   ; return for another iteration
111
112
113 endloop
114
115 sto r0 r3 0    ; write the value of product
116 hlt
117
118
119
120
121
122
123
124
125
126
127
128
129
130
131
132
133
134
135
136
137 }
    
```


What now?

```

loa r1 r0 0 ; get a value for a
loa r2 r0 0 ; get a value for b
add r3 r0 r0 ; result = 0;

loop
ble r1 r0 endloop ; test if a <= 0
add r3 r3 r2 ; result += b;
sbc r1 r1 1 ; a--;
blt r0 r1 loop ; return for another iteration

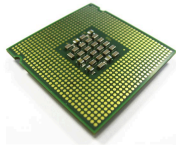endloop
sto r0 r3 0 ; write the value of product
hlt ; halt
end
    
```



One last note on CS41B

Instruction View

```

0000 : I/O
0002 : 9400 loa r1 r0
0004 : 9800 loa r2 r0
0006 : cc00 add r3 r0 r0
0008 : 7106 bge r0 r1 0010
000a : cf80 add r3 r3 r2
000c : f501 sbc r1 r1 1
000e : 61fa blt r0 r1 000a
0010 : 8300 sto r0 r3
0012 : 1000 hlt
    
```

memory address
binary representation of code
instructions (assembly code)

How do we get this?

Encoding assembly instructions

4	2	2	2	6
opcode	dest	src0	src1	unused

4	2	2	8
opcode	dest	src0	argument

Instruction View

```

0000 : I/O
0002 : 9400 loa r1 r0
0004 : 9800 loa r2 r0
0006 : cc00 add r3 r0 r0
0008 : 7106 bge r0 r1 0010
000a : cf80 add r3 r3 r2
000c : f501 sbc r1 r1 1
000e : 61fa blt r0 r1 000a
0010 : 8300 sto r0 r3
0012 : 1000 hlt
    
```

1001 0100 0000 0000

1001 1000 0000 0000


1100 1100 0000 0000

opcode dest src0 src1

What now?

```

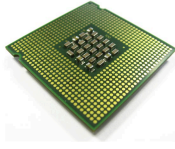1001 0100 0000 0000
1001 1000 0000 0000
1100 1100 0000 0000
    
```



Review: binary addition

$$\begin{array}{r} 01010 \\ + 01111 \\ \hline ? \end{array}$$

Do the binary addition, making sure to keep track of the carries.
Assume unsigned numbers for now.

Review: binary addition

$$\begin{array}{r} 1110 \\ 01010 \\ + 01111 \\ \hline 11001 \end{array}$$

Just to be sure, what are these numbers in decimal?

Review: binary addition

$$\begin{array}{r} 1110 \\ 01010 \quad 10 \\ + 01111 \quad 15 \\ \hline 11001 \quad 25 \end{array}$$

We saw before, that we can view this problem recursively. How?

```

fun addAsListsBinary 0 nil      nil      = nil
| addAsListsBinary c nil      nil      = [c]
| addAsListsBinary c x1      nil      = addAsListsBinary c x1 [0]
| addAsListsBinary c nil      y1      = addAsListsBinary c [0] y1
| addAsListsBinary c (x::xs) (y::ys) =
  let
    val total = c + x + y
  in
    if total >= 2 then (* check if there's a carry *)
      (total - 2)::addAsListsBinary 1 xs ys
    else
      total::addAsListsBinary 0 xs ys
  end;

```

```

fun addAsListsBinary 0 nil nil = nil
| addAsListsBinary c nil nil = [c]
| addAsListsBinary c xl nil = addAsListsBinary c xl [0]
| addAsListsBinary c nil yl = addAsListsBinary c [0] yl
| addAsListsBinary c (x::xs) (y::ys) =
  let
    val total = c + x + y
  in
    if total >= 2 then (* check if there's a carry *)
      (total - 2)::addAsListsBinary 1 xs ys
    else
      total::addAsListsBinary 0 xs ys
  end;

```

handle a digit at a time

```

fun addAsListsBinary 0 nil nil = nil
| addAsListsBinary c nil nil = [c]
| addAsListsBinary c xl nil = addAsListsBinary c xl [0]
| addAsListsBinary c nil yl = addAsListsBinary c [0] yl
| addAsListsBinary c (x::xs) (y::ys) =
  let
    val total = c + x + y
  in
    if total >= 2 then (* check if there's a carry *)
      (total - 2)::addAsListsBinary 1 xs ys
    else
      total::addAsListsBinary 0 xs ys
  end;





```

generate two pieces of information

- output bit
- carry bit

A recursive component

Adding with components

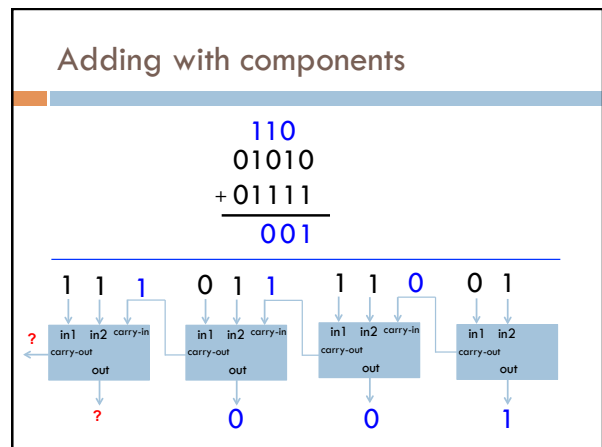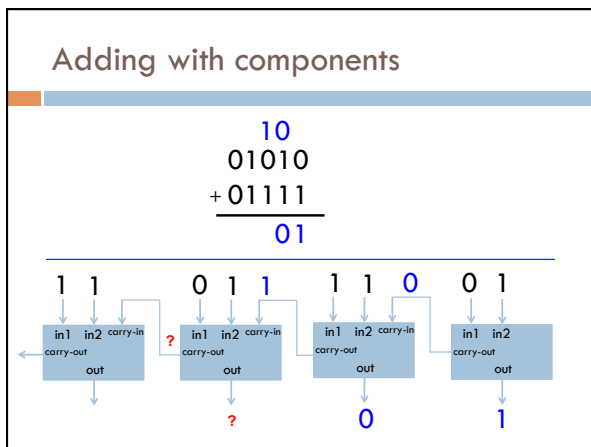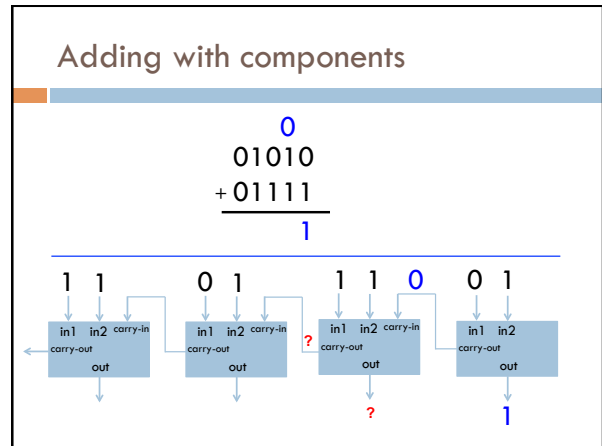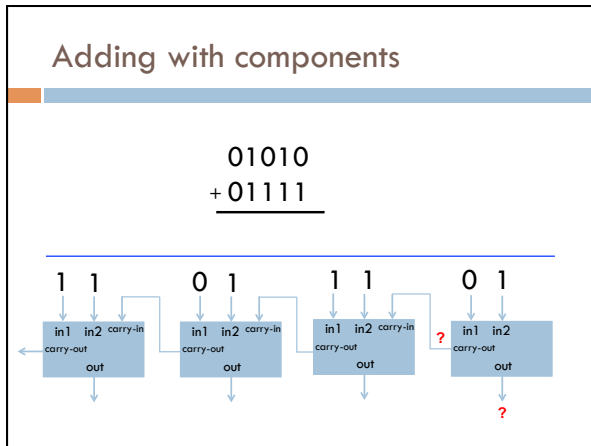

Adding with components

$$\begin{array}{r}
 1110 \\
 01010 \\
 + 01111 \\
 \hline
 11001
 \end{array}$$

Implementing the component

What goes on inside the component?

Implementing the component

```

let
  val total = c + x + y
in
  if total >= 2 then (* check if there's a carry *)
    (total - 2)::addAsListsBinary 1 xs ys
  else
    total::addAsListsBinary 0 xs ys
end;

```


Current implementation uses addition!

Implementing the component

in1	in2	carry-in	out	carry-out
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

What are the outputs?

Implementing the component

 

in1	in2	carry-in	out	carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Another implementation

```

fun addAsListsBinary 0 nil nil = nil
| addAsListsBinary c nil nil = [c]
| addAsListsBinary c xl nil = addAsListsBinary c xl [0]
| addAsListsBinary c nil yl = addAsListsBinary c [0] yl
| addAsListsBinary c (x::xs) (y::ys) =
  if x = 1 andalso y = 1 andalso c = 1 then
    1::(addAsListsBinary 1 xs ys)
  else if (x = 1 andalso y = 1) orelse
    (x = 1 andalso c = 1) orelse
    (y = 1 andalso c = 1) then
    0::(addAsListsBinary 1 xs ys)
  else if x = 1 orelse y = 1 orelse c = 1 then
    1::(addAsListsBinary 0 xs ys)
  else
    0::(addAsListsBinary 0 xs ys);
  
```

- Don't use addition anymore
- Translated the problem into a boolean logic problem

What are some boolean operators?


A	B	A and B	A or B	not A
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0

What are some boolean operators?


A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

Gates


not




xor




and




nand

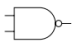

or



nor

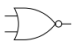



Gates have inputs and outputs

- values are 0 or 1

Are **hardware** components!

Gates as hardware

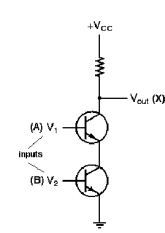


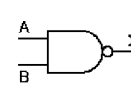


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Utilizing gates


A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

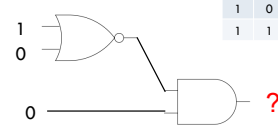


not




xor

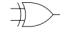


and

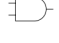


nand



or




nor




Utilizing gates


A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

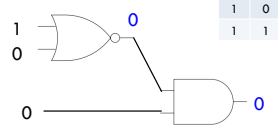


not




xor

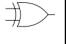


and




nand



or

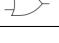

nor



Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

not xor

and nand

or nor

Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

When is this circuit 1?

not xor

and nand

or nor

Utilizing gates

in1	in2	in3	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Designing more interesting circuits

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

in1	in2	in3	OUT
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Design a circuit for this


not xor

and nand

or nor


Designing more interesting circuits

in1	in2	in3	OUT
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

 

Back to addition...

in1	in2	carry-in	carry-out	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

A half-adder: no carry-in

A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


A half-adder: no carry-in

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


Hint: solve each output bit independently

Design a circuit for this

 


A half-adder: no carry-in


A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


Implementing a full adder

 

Implementing a full adder

 


Implementing the component

 

What goes on inside the component?

Implementing the component

 


Ripple carry adder

To implement an n -bit adder, we chain together n full-adders, each adder handles one bit position

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

Adder for adding 4-bit numbers

 


Ripple carry adder

To implement an n -bit adder, we chain together n full-adders, each adder handles one bit position

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

Adder for adding 4-bit numbers

 

Signed addition

$$0010$$

$$+ 1110$$

?

Do the binary addition, making sure to keep track of the carries.
Assume signed numbers for now.

Signed addition

throw away last carry bit →

$$\begin{array}{r} 1110 \\ 0010 \\ + 1110 \\ \hline 0000 \end{array}$$

Is that right?
What numbers are these?

Signed addition

$$\begin{array}{r} 1110 \\ 0010 \quad 2 \\ + 1110 \quad -2 \\ \hline 0000 \quad 0 \end{array}$$

Ripple carry adder will work for signed and unsigned numbers

Subtraction



$$\begin{array}{r} 0010 \\ - 1110 \\ \hline \end{array}$$

We can solve this doing addition

Subtraction

$$\begin{array}{r} 0010 \\ - 1110 \\ \hline \end{array} \quad \begin{array}{c} \rightarrow \\ \text{flip bits} \\ \text{and add 1} \end{array} \quad \begin{array}{r} 0010 \\ 0010 \\ \hline 0100 \end{array}$$

Do addition!

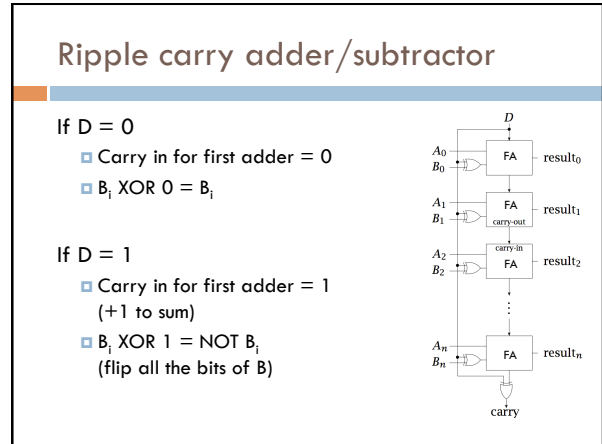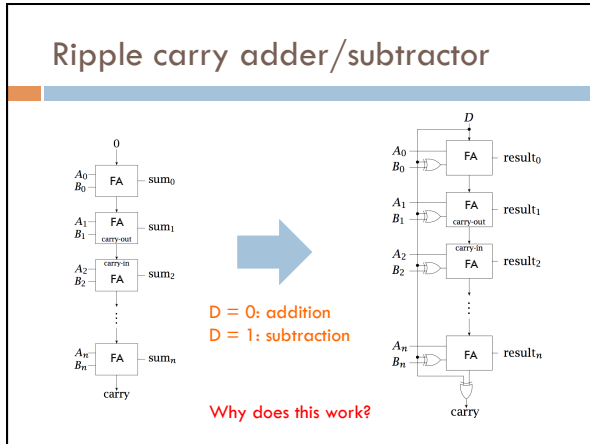

C, N, Z and V bits

In addition to the sum, we often also calculate some other useful information:

- ▣ C: carry out bit of the adder
- ▣ Z: 1 if the total result is zero, 0 otherwise
- ▣ N: sign bit of the result
- ▣ V: if there was "signed overflow": the result cannot be represented with the number of bits we're using

What are the cases where signed overflow can occur?

V bit

V: if there was "signed overflow": the result cannot be represented with the number of bits we're using

- Adding two positive numbers (too big positive)
- Subtracting a negative number from a positive number (too big positive)
- Adding two negative numbers (too big negative)
- Subtracting a positive number from a negative number (too big negative)

Detecting overflow

$$\begin{array}{r} 0011 \\ + 0101 \\ \hline \end{array}$$

Add these (as signed numbers).
Does overflow occur?

Detecting overflow

$$\begin{array}{r} 111 \\ 0011 \\ + 0101 \\ \hline 1000 \end{array}$$

Yes. How do we detect it?

Detecting overflow

$$\begin{array}{r} 111 \\ 0011 \\ + 0101 \\ \hline 1000 \end{array}$$

- Added two positive numbers and got a negative
- In general: if the sign bits are the same (**of the numbers we end up adding**), but the higher order bit of result is different = overflow

Detecting overflow

$$\begin{array}{r} 0011 \\ - 1001 \\ \hline \end{array}$$

Subtract these (as signed numbers).
Does overflow occur?

Detecting overflow

$$\begin{array}{r} 000 \\ 0011 \\ - 1001 \\ \hline 1010 \end{array}$$

Yes. How do we detect it?

Detecting overflow

$$\begin{array}{r} 000 \\ 0011 \\ - 1001 \\ \hline 1010 \end{array}$$

- Subtracted a negative number from a positive, should have been positive
- In general: if the sign bits are the different (**of the numbers we end up subtracting**), but the higher order bit of result is different = overflow

Detecting overflow

$$\begin{array}{r} 100 \\ 0011 \\ - 1101 \\ \hline 0110 \end{array}$$

- Subtracted a negative number from a positive
- In general: if the sign bits are the same (**of the numbers we end up adding**), but the higher order bit of result is different = overflow

Python basics