


### Admin


Assignment 4 due Monday at 11:59pm

Assignment 5 posted soon

- due Friday March 11, at 5pm (before spring break!)

Academic Honesty: Thanks!

 

 

### After intro CS

A diagram showing a road with several cars (yellow, blue, and purple) moving across it. An orange arrow points from the road to a code snippet. The code snippet is a Java class definition for a Frog:

```

import javax.swing.*;
public class Frog {
    // height of the frog image
    private static final double FROG_HEIGHT = 48;
    // This should refer to the image of the frog. Note that it is not
    // initialized by // the code we loop provided.
    private VisibleImage frogImage;
    public Frog() {
    }
    public boolean overlaps(VisibleImage vehicleImage) {
        return false; // YOU NEED TO CHANGE THIS!
    }
    public void killed() {
    }
    public void reincarnate() {
    }
    public void hopToward(Location point) {
    }
    public boolean isAlive() {
        return false; // YOU NEED TO CHANGE THIS!
    }
}
    
```

### After 5 weeks of cs52

A diagram showing the translation of Java code to assembly code. On the left is the Java code from the previous slide. An orange arrow points to the assembly code on the right:

```

loop
    lda r1 r0 0      ; get a value for a
    lda r2 r0 0      ; get a value for b
    add r3 r0 r0     ; result = 0;
    ble r1 r0 endloop ; test if a <= 0
    add r3 r3 r2     ; result += b;
    sbc r1 r1 1      ; a--;
    bit r0 r1 loop   ; return for another iteration
endloop
sto r0 r3 0        ; write the value of product
hit
end
    
```

### What now?

A diagram showing assembly code and a CPU chip. On the left is the assembly code from the previous slide. An orange arrow points to a photograph of a green CPU chip.

```

lda r1 r0 0      ; get a value for a
lda r2 r0 0      ; get a value for b
add r3 r0 r0     ; result = 0;
ble r1 r0 endloop ; test if a <= 0
add r3 r3 r2     ; result += b;
sbc r1 r1 1      ; a--;
bit r0 r1 loop   ; return for another iteration
endloop
sto r0 r3 0        ; write the value of product
hit
end
    
```

### One last note on CS41B

Instruction View

```

0000 : I/O
0002 : 9400 loa r1 r0
0004 : 9800 loa r2 r0
0006 : cc00 add r3 r0 r0
0008 : 7106 bge r0 r1 0010
000a : cf80 add r3 r3 r2
000c : f501 sbc r1 r1 1
000e : 61fa blt r0 r1 000a
0010 : 8300 sto r0 r3
0012 : 1000 hlt
    
```

memory address      binary representation of code      instructions (assembly code)

How do we get this?

### Encoding assembly instructions

4	2	2	2	6
opcode	dest	src0	src1	unused

4	2	2	8
opcode	dest	src0	argument

Instruction View

```

0000 : I/O
0002 : 9400 loa r1 r0
0004 : 9800 loa r2 r0
0006 : cc00 add r3 r0 r0
0008 : 7106 bge r0 r1 0010
000a : cf80 add r3 r3 r2
000c : f501 sbc r1 r1 1
000e : 61fa blt r0 r1 000a
0010 : 8300 sto r0 r3
0012 : 1000 hlt
    
```


1001 0100 0000 0000  
 1001 1000 0000 0000  
 1100 1100 0000 0000

opcode dest src0 src1
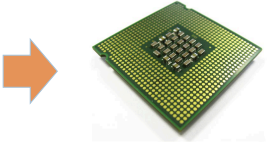
### What now?

```

1001 0100 0000 0000
1001 1000 0000 0000
1100 1100 0000 0000
    
```



### Review: binary addition

$$\begin{array}{r}
 01010 \\
 + 01111 \\
 \hline
 ?
 \end{array}$$

Do the binary addition, making sure to keep track of the carries. Assume unsigned numbers for now.

### Review: binary addition

$$\begin{array}{r}
 1110 \\
 01010 \\
 + 01111 \\
 \hline
 11001
 \end{array}$$

Just to be sure, what are these numbers in decimal?

### Review: binary addition

$$\begin{array}{r}
 1110 \\
 01010 \\
 + 01111 \\
 \hline
 11001
 \end{array}
 \begin{array}{l}
 10 \\
 15 \\
 25
 \end{array}$$

We saw before, that we can view this problem recursively. How?

### SML: Binary addition

```

fun addAsListsBinary 0 [] [] = []
| addAsListsBinary c [] [] = [c]
| addAsListsBinary c xl [] = addAsListsBinary c xl [0]
| addAsListsBinary c [] yl = addAsListsBinary c [0] yl
| addAsListsBinary c (x::xs) (y::ys) =
  let
    val total = c + x + y
  in
    if total >= 2 then (* check if there's a carry *)
      (total - 2)::addAsListsBinary 1 xs ys
    else
      total::addAsListsBinary 0 xs ys
  end;

```

### SML: Binary addition

```

fun addAsListsBinary 0 [] [] = []
| addAsListsBinary c [] [] = [c]
| addAsListsBinary c xl [] = addAsListsBinary c xl [0]
| addAsListsBinary c [] yl = addAsListsBinary c [0] yl
| addAsListsBinary c (x::xs) (y::ys) =
  let
    val total = c + x + y
  in
    if total >= 2 then (* check if there's a carry *)
      (total - 2)::addAsListsBinary 1 xs ys
    else
      total::addAsListsBinary 0 xs ys
  end;

```

$$\begin{array}{r}
 1110 \\
 01010 \\
 + 01111 \\
 \hline
 11001
 \end{array}$$

handle a digit at a time

### SML: Binary addition


```

fun addAsListsBinary 0 [] [] = []
  | addAsListsBinary c [] [] = [c]
  | addAsListsBinary c x1 [] = addAsListsBinary c x1 [0]
  | addAsListsBinary c [] y1 = addAsListsBinary c [0] y1
  | addAsListsBinary c (x::xs) (y::ys) =
    let
      val total = c + x + y
    in
      if total >= 2 then (* check if there's a carry *)
        (total - 2)::addAsListsBinary 1 xs ys
      else
        total::addAsListsBinary 0 xs ys
    end;


```

generate two pieces of information  
 - output bit  
 - carry bit


### A recursive component




 


### Adding with components

 


### Adding with components

 

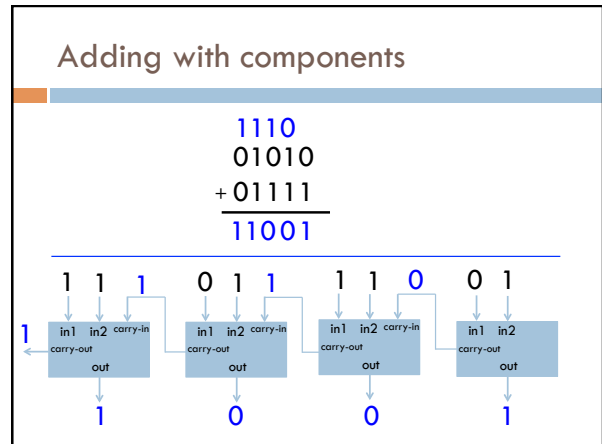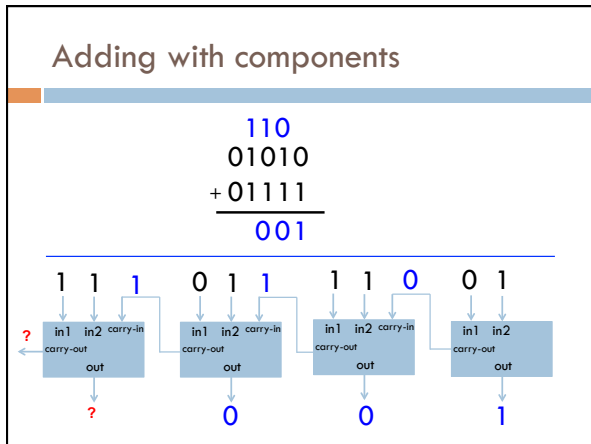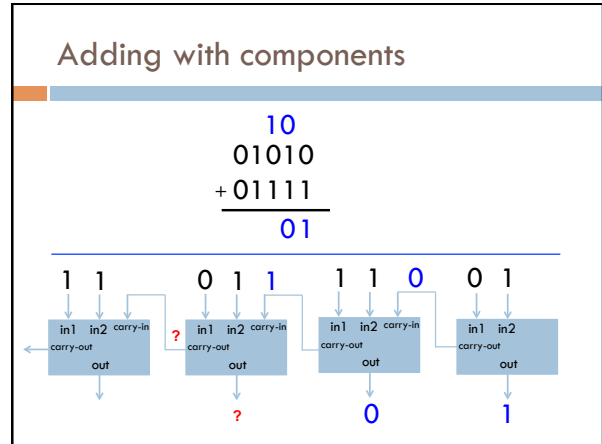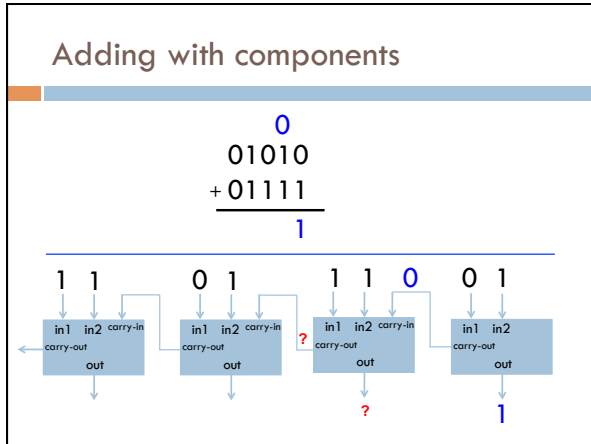

### Implementing the component

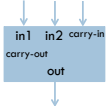

What goes on inside the component?


### Implementing the component

```


let
  val total = c + x + y
in
  if total >= 2 then (* check if there's a carry *)
    (total - 2)::addAsListsBinary 1 xs ys
  else
    total::addAsListsBinary 0 xs ys
end;

```

Current implementation uses addition!




### Implementing the component

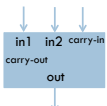

in1	in2	carry-in	out	carry-out
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

What are the outputs?

### Implementing the component

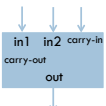

in1	in2	carry-in	out	carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Another implementation

```

fun addAsListsBinary 0 [] [] = []
| addAsListsBinary c [] [] = [c]
| addAsListsBinary c xl [] = addAsListsBinary c xl [0]
| addAsListsBinary c [] yl = addAsListsBinary c [0] yl
| addAsListsBinary c (x::xs) (y::ys) =
  if x = 1 andalso y = 1 andalso c = 1 then
    1::(addAsListsBinary 1 xs ys)
  else if (x = 1 andalso y = 1) orelse
    (x = 1 andalso c = 1) orelse
    (y = 1 andalso c = 1) then
    0::(addAsListsBinary 1 xs ys)
  else if x = 1 orelse y = 1 orelse c = 1 then
    1::(addAsListsBinary 0 xs ys)
  else
    0::(addAsListsBinary 0 xs ys);
  
```

- Don't use addition anymore
- Translated the problem into a boolean logic problem


## What are some boolean operators?

A	B	A and B	A or B	not A
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0

## What are some boolean operators?

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

## Gates

 

Gates have inputs and outputs

- values are 0 or 1

They are **hardware** components!



### Gates as hardware

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

### Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

not

and

or

xor

nand

nor

### Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

not

and

or

xor

nand

nor

### Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

not

and

or

xor

nand

nor

### Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

When is this circuit 1?

not

and

or

xor

nand

nor

### Utilizing gates

in1	in2	in3	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

### Designing more interesting circuits

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

in1	in2	in3	OUT
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Design a circuit for this

not

and

or

xor

nand


nor

### Designing more interesting circuits

in1	in2	in3	OUT
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

### Back to addition...

in1	in2	carry-in	carry-out	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

### A half-adder: no carry-in

A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


### A half-adder: no carry-in

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


Hint: solve each output bit independently





Design a circuit for this

 

### A half-adder: no carry-in

A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

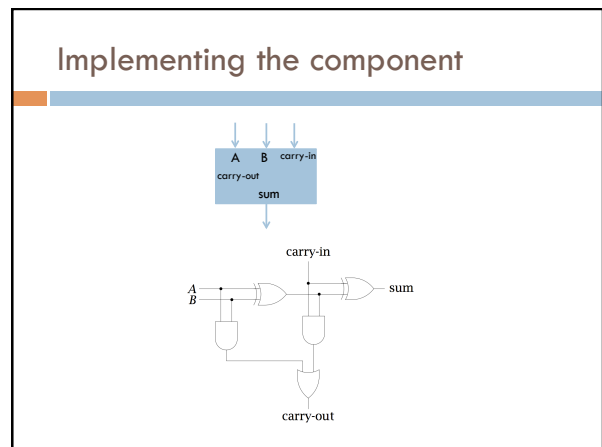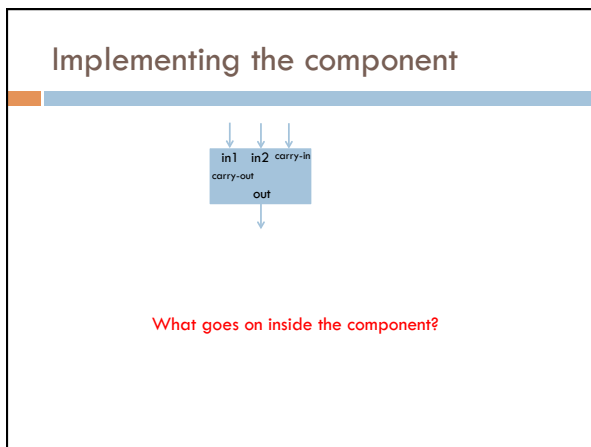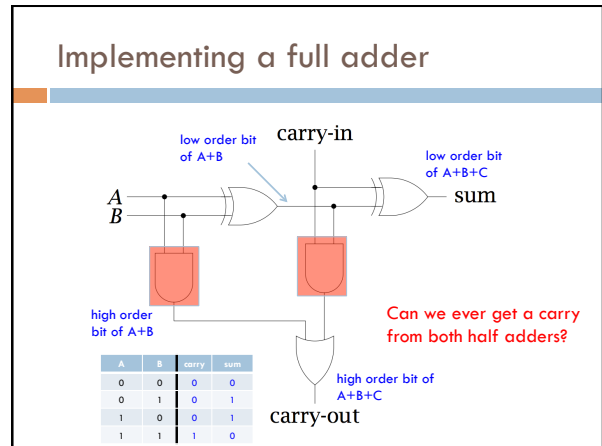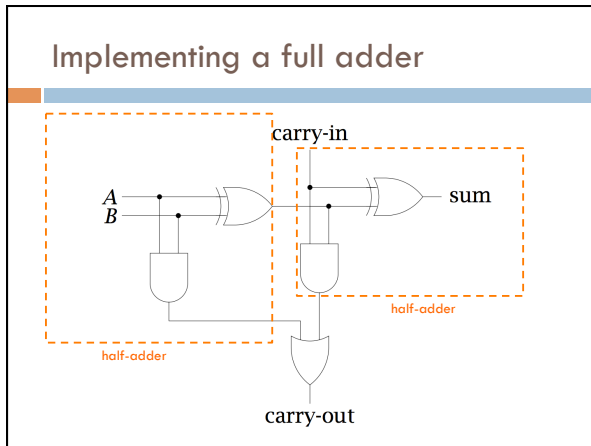


### Ripple carry adder

To implement an  $n$ -bit adder, we chain together  $n$  full-adders, each adder handles one bit position

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

Adder for adding 4-bit numbers

 


### Ripple carry adder

To implement an  $n$ -bit adder, we chain together  $n$  full-adders, each adder handles one bit position

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

Adder for adding 4-bit numbers

 

### Signed addition

$$\begin{array}{r} 0010 \\ + 1110 \\ \hline ? \end{array}$$

Do the binary addition, making sure to keep track of the carries.  
Assume **signed** numbers for now.

### Signed addition

throw away last carry bit  $\rightarrow$

$$\begin{array}{r} 1110 \\ 0010 \\ + 1110 \\ \hline 0000 \end{array}$$

Is that right?  
What numbers are these?

### Signed addition

$$\begin{array}{r}
 1110 \\
 0010 \quad 2 \\
 + 1110 \quad -2 \\
 \hline
 0000 \quad 0
 \end{array}$$

Ripple carry adder will work for signed and unsigned numbers

### Subtraction

$$\begin{array}{r}
 0010 \\
 - 1110 \\
 \hline
 \end{array}$$

How can we solve this with addition?


### Subtraction

$$\begin{array}{r}
 0010 \\
 - 1110 \\
 \hline
 \end{array}
 \quad \rightarrow \quad
 \begin{array}{r}
 0010 \\
 0010 \\
 \hline
 0100
 \end{array}$$

flip bits and add 1

Do addition!

### Ripple carry adder/subtractor

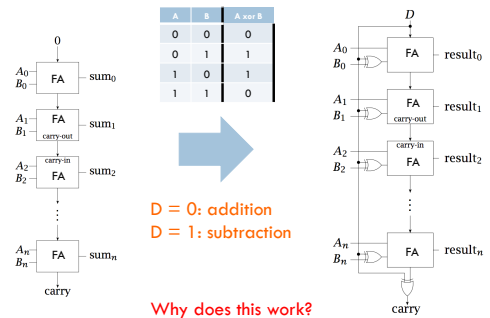


## Ripple carry adder/subtractor

If  $D = 0$

- Carry in for first adder = 0
- $B_i \text{ XOR } 0 = B_i$

If  $D = 1$

 - Carry in for first adder = 1  
(+1 to sum)
- $B_i \text{ XOR } 1 = \text{NOT } B_i$   
(flip all the bits of B)



## C, N, Z and V bits

In addition to the sum, we often also calculate some other useful information:

- C: carry out bit of the adder
- Z: 1 if the total result is zero, 0 otherwise
- N: sign bit of the result
- V: if there was "signed overflow": the result cannot be represented with the number of bits we're using

What are the cases where signed overflow can occur?

## V bit

V: if there was "signed overflow": the result cannot be represented with the number of bits we're using

- Adding two positive numbers (too big positive)
- Subtracting a negative number from a positive number (too big positive)
- Adding two negative numbers (too big negative)
- Subtracting a positive number from a negative number (too big negative)

## Detecting overflow

$$\begin{array}{r} 0011 \\ + 0101 \\ \hline \end{array}$$

Add these (as signed numbers).  
Does overflow occur?

## Detecting overflow

$$\begin{array}{r} 111 \\ 0011 \\ + 0101 \\ \hline 1000 \end{array}$$

Yes. How do we detect it?

## Detecting overflow

$$\begin{array}{r} 111 \\ 0011 \\ + 0101 \\ \hline 1000 \end{array}$$

- Added two positive numbers and got a negative
- In general: if the sign bits are the same (**of the numbers we end up adding**), but the higher order bit of the result is different = overflow

## Detecting overflow

$$\begin{array}{r} 0011 \\ - 1001 \\ \hline \end{array}$$

Subtract these (as signed numbers).  
Does overflow occur?

## Detecting overflow

$$\begin{array}{r} 000 \\ 0011 \\ - 1001 \\ \hline 1010 \end{array}$$

Yes. How do we detect it?



### Detecting overflow

$$\begin{array}{r}
 000 \\
 0011 \\
 - 1001 \\
 \hline
 1010
 \end{array}
 \quad \rightarrow \quad
 \begin{array}{r}
 111 \\
 0011 \\
 + 0111 \\
 \hline
 1011
 \end{array}$$

- Subtracted a negative number from a positive, should have been positive
- In general: if the sign bits are the same (**of the numbers we end up adding**), but the higher order bit of the result is different = overflow

### Python basics