

CIRCUITS

David Kauchak
CS 52 – Spring 2017

Admin


- Assignment 5
- Assignment 6 out soon!
- Survey


Examples

The Logisim circuit examples can be found at:


<http://www.cs.pomona.edu/~dkauchak/classes/cs52/examples/logisim/>

Diving into your computer



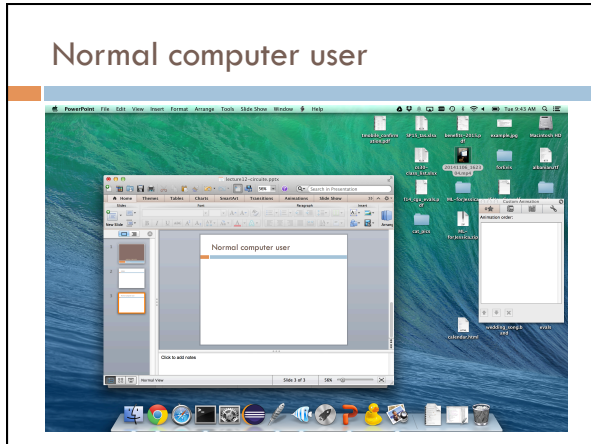

After intro CS

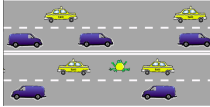

```

1=) import objectDraw.*
2
3 public class Frog {
4     // height of the frog image
5     private static final double FROG_HEIGHT = 48;
6
7     // This should refer to the image of the frog. Note that it is not
8     // initialized by
9     // the code we loop provided.
10    private VisibleImage frogImage;
11
12    public Frog() {
13    }
14
15    public boolean overlaps(VisibleImage vehicleImage) {
16        return false; // YOU NEED TO CHANGE THIS!
17    }
18
19    public void killed() {
20    }
21
22    public void reanimate() {
23    }
24
25    public void hopToward(Location point) {
26    }
27
28    public boolean isAlive() {
29        return false; // YOU NEED TO CHANGE THIS!
30    }
31
32 }
                
```

After 5 weeks of cs52

```

1=) import objectDraw.*
2
3 public class Frog {
4     // height of the frog image
5     private static final double FROG_HEIGHT = 48;
6
7     // This should refer to the image of the frog. Note that it is not
8     // initialized by
9     // the code we loop provided.
10    private VisibleImage frogImage;
11
12    public Frog() {
13    }
14
15    public boolean overlaps(VisibleImage vehicleImage) {
16        return false; // YOU NEED TO CHANGE THIS!
17    }
18
19    public void killed() {
20    }
21
22    public void reanimate() {
23    }
24
25    public void hopToward(Location point) {
26    }
27
28    public boolean isAlive() {
29        return false; // YOU NEED TO CHANGE THIS!
30    }
31
32 }
                
```

➔

```


loop
    l0a r1 r0 0      ; get a value for a
    l0a r2 r0 0      ; get a value for b
    add r3 r0 r0     ; result = 0;
    ble r1 r0 endloop ; test if a <= 0
    add r3 r3 r2     ; result += b;
    sbc r1 r1 1      ; a--;
    bit r0 r1 loop   ; return for another iteration
endloop
sto r0 r3 0        ; write the value of product
hit
end
                
```

What now?

```

loop
    l0a r1 r0 0      ; get a value for a
    l0a r2 r0 0      ; get a value for b
    add r3 r0 r0     ; result = 0;
    ble r1 r0 endloop ; test if a <= 0
    add r3 r3 r2     ; result += b;
    sbc r1 r1 1      ; a--;
    bit r0 r1 loop   ; return for another iteration
endloop
sto r0 r3 0        ; write the value of product
hit
end
                
```

➔

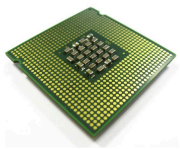

Quick recap

$$\begin{array}{r} 01010 \\ + 01111 \\ \hline \end{array}$$

Quick recap

$$\begin{array}{r} 1110 \\ 01010 \\ + 01111 \\ \hline 11001 \end{array}$$

SML: Binary addition

```

fun addAsListsBinary 0 [] [] = []
| addAsListsBinary c [] [] = [c]
| addAsListsBinary c xl [] = addAsListsBinary c xl [0]
| addAsListsBinary c [] yl = addAsListsBinary c [0] yl
| addAsListsBinary c (x::xs) (y::ys) =
  let
    val total = c + x + y
  in
    if total >= 2 then (* check if there's a carry *)
      (total - 2)::addAsListsBinary 1 xs ys
    else
      total::addAsListsBinary 0 xs ys
  end;

```

SML: Binary addition

```

fun addAsListsBinary 0 [] [] = []
| addAsListsBinary c [] [] = [c]
| addAsListsBinary c xl [] = addAsListsBinary c xl [0]
| addAsListsBinary c [] yl = addAsListsBinary c [0] yl
| addAsListsBinary c (x::xs) (y::ys) =
  let
    val total = c + x + y
  in
    if total >= 2 then (* check if there's a carry *)
      (total - 2)::addAsListsBinary 1 xs ys
    else
      total::addAsListsBinary 0 xs ys
  end;

```

handle a digit at a time

SML: Binary addition


```

fun addAsListsBinary 0 [] [] = []
  | addAsListsBinary c [] [] = [c]
  | addAsListsBinary c x1 [] = addAsListsBinary c x1 [0]
  | addAsListsBinary c [] y1 = addAsListsBinary c [0] y1
  | addAsListsBinary c (x::xs) (y::ys) =
    let
      val total = c + x + y
    in
      if total >= 2 then (* check if there's a carry *)
        (total - 2)::addAsListsBinary 1 xs ys
      else
        total::addAsListsBinary 0 xs ys
    end;


```

generate two pieces of information
 - output bit
 - carry bit


A recursive component




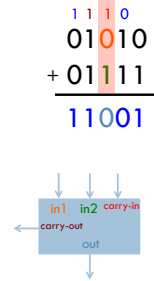


Adding with components

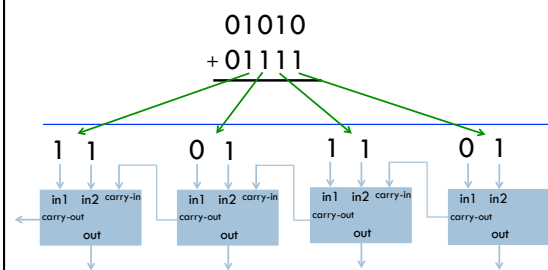


Adding with components

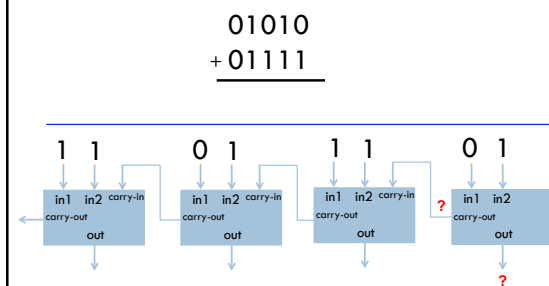

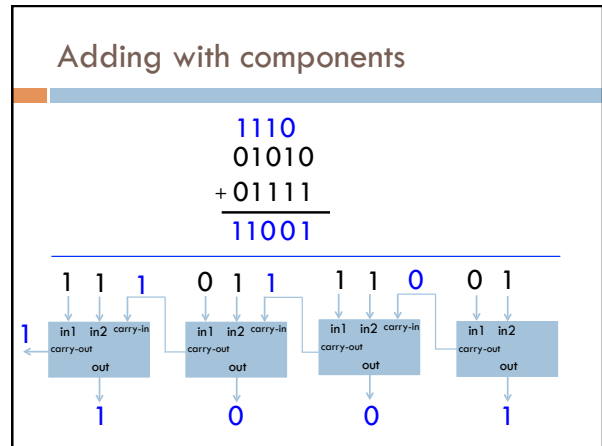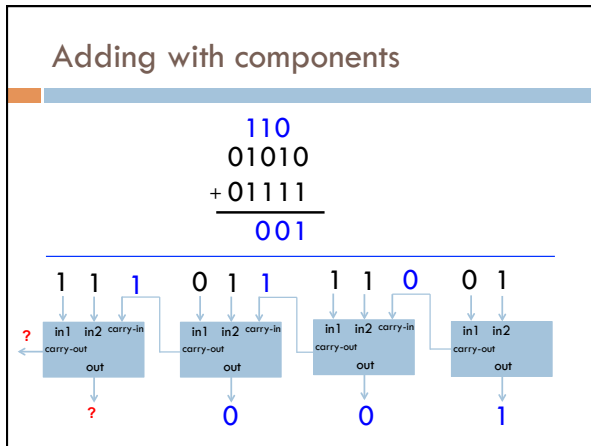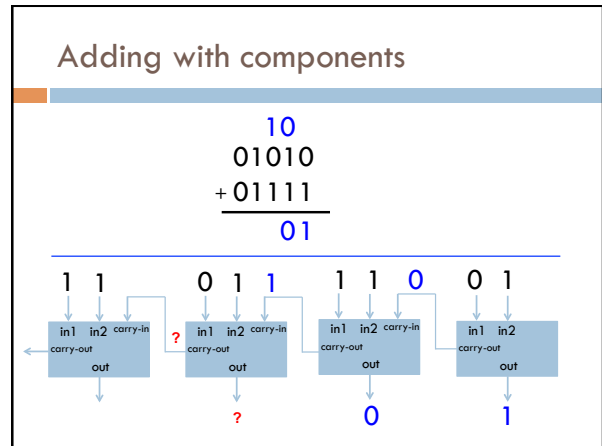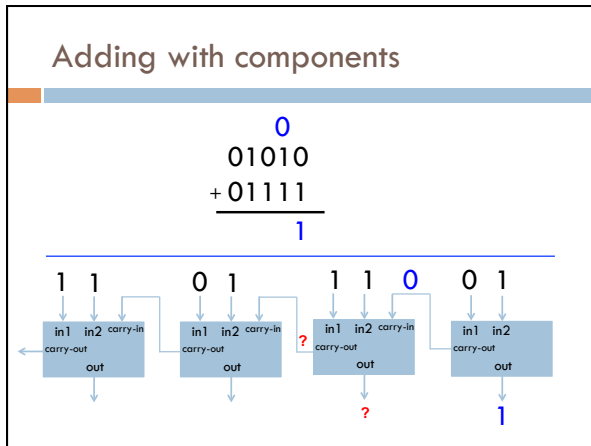

Implementing the component

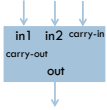

What goes on inside the component?


Implementing the component

```


let
  val total = c + x + y
in
  if total >= 2 then (* check if there's a carry *)
    (total - 2)::addAsListsBinary 1 xs ys
  else
    total::addAsListsBinary 0 xs ys
end;

```

Current implementation uses addition!




Implementing the component

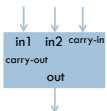

in1	in2	carry-in	out	carry-out
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

What are the outputs?

Implementing the component

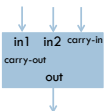

in1	in2	carry-in	out	carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Another implementation

```

fun addAsListsBinary 0 [] [] = []
| addAsListsBinary c [] [] = [c]
| addAsListsBinary c xl [] = addAsListsBinary c xl [0]
| addAsListsBinary c [] yl = addAsListsBinary c [0] yl
| addAsListsBinary c (x::xs) (y::ys) =
  if x = 1 andalso y = 1 andalso c = 1 then
    1::(addAsListsBinary 1 xs ys)
  else if (x = 1 andalso y = 1) orelse
    (x = 1 andalso c = 1) orelse
    (y = 1 andalso c = 1) then
    0::(addAsListsBinary 1 xs ys)
  else if x = 1 orelse y = 1 orelse c = 1 then
    1::(addAsListsBinary 0 xs ys)
  else
    0::(addAsListsBinary 0 xs ys);
  
```

- Don't use addition anymore
- Translated the problem into a boolean logic problem


What are some boolean operators?

A	B	A and B	A or B	not A
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0

What are some boolean operators?

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

Gates

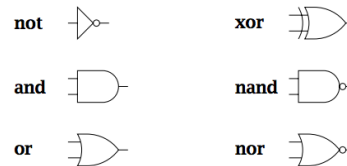

Gates have inputs and outputs

- values are 0 or 1

They are **hardware** components!

Gates as hardware

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

not

and

or

xor

nand

nor

Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

not

and

or

xor

nand

nor

Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

not

and

or

xor

nand

nor

Utilizing gates

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

When is this circuit 1?

not

and

or

xor

nand

nor

Utilizing gates

in1	in2	in3	OUT
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Designing more interesting circuits

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

in1	in2	in3	OUT
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Design a circuit for this

not

and

or

xor

nand

nor

Designing more interesting circuits

in1	in2	in3	OUT
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Designing more interesting circuits

in1	in2	in3	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Design a circuit for this

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0

not

and

or

xor

nand

nor

Minterm expansion

A failsafe way to design a circuit...

in1	in2	in3	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Minterm expansion

A failsafe way to design a circuit...


in1	in2	in3	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

All these should be 1 and everything else 0

Minterm expansion


When will this and-gate be 1?

Minterm expansion

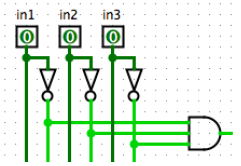


Only when $in1=0, in2=0, in3=0$

Minterm expansion

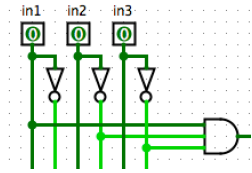


When will this and-gate be 1?

Minterm expansion

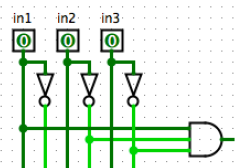

Only when $in1=1, in2=0, in3=0$

Minterm expansion

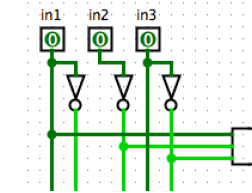

Does this help us?

Minterm expansion

in1	in2	in3	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Only these three inputs can be true!

Minterm expansion

in1	in2	in3	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

How do we combine these?

Minterm expansion

in1	in2	in3	OUT
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Or-gate!

Back to addition...

in1	in2	carry-in	carry-out	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

A half-adder: no carry-in

A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



A half-adder: no carry-in

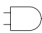

A	B	A and B	A or B	not A	A nand B	A nor B	A xor B
0	0	0	0	1	1	1	0
0	1	0	1	1	1	0	1
1	0	0	1	0	1	0	1
1	1	1	1	0	0	0	0



A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Hint: solve each output bit independently

Design a circuit for this


not  xor 

and  nand 


or  nor 

A half-adder: no carry-in


A	B	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

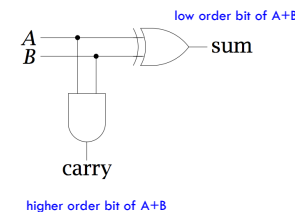


Implementing a full adder

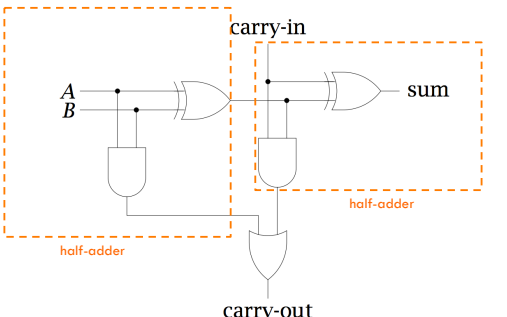

Implementing a full adder

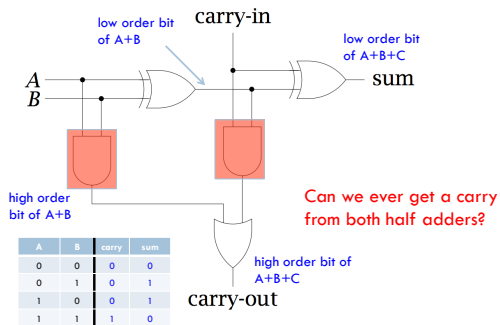


Implementing the component

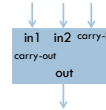

What goes on inside the component?

Implementing the component

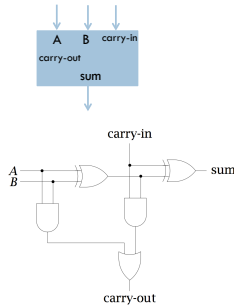


Ripple carry adder

To implement an n -bit adder, we chain together n full adders, each adder handles one bit position

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

Adder for adding 4-bit numbers

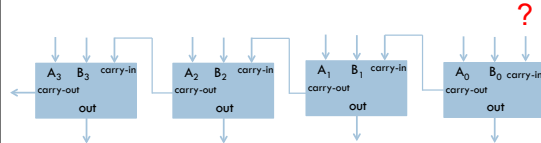


Ripple carry adder

To implement an n -bit adder, we chain together n full-adders, each adder handles one bit position

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

Adder for adding 4-bit numbers

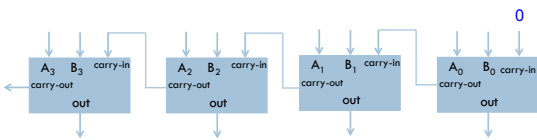


Look at ripple carry adder example

Many circuits

- ▣ half-adder
- ▣ full-adder (using half-adders)
- ▣ ripple-carry adder (using full-adders)

Simulator basics


Mystery circuit

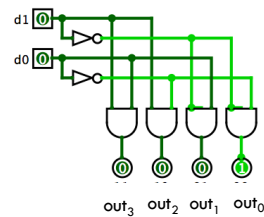

d_1	d_0	out_0	out_1	out_2	out_3
0	0				
0	1				
1	0				
1	1				


What does this circuit do?

2-bit decoder

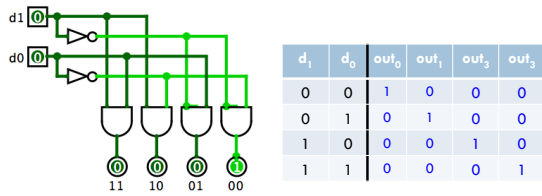


Sends '1' along one of the output lines

2-bit decoder*

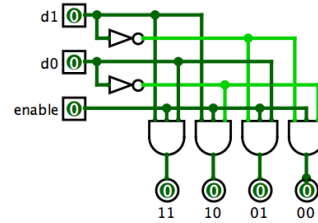

What does the extra input do?

2-bit decoder*

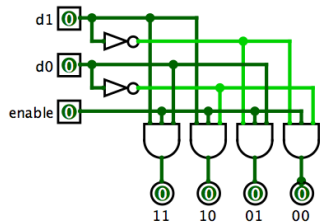

When 0, doesn't select any lines, when 1, functions normally

3-bit decoder

3 inputs

How many output lines?

3-bit decoder


3 inputs

8 output lines

Could make from scratch


Better idea: reuse 2-bit decoders

3-bit decoder

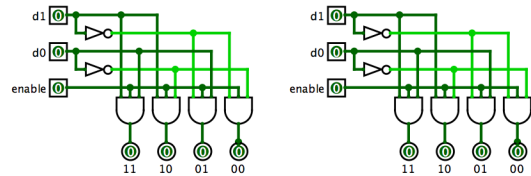


Could we use two 2-bit decoders?

3-bit decoder

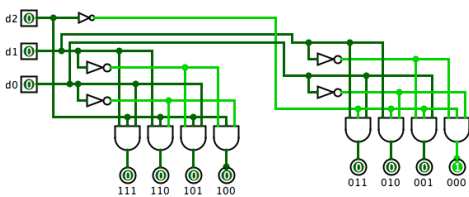

d2 gets sent to the enable of the two 2-bit decoders. One as normal and one negated.

3-bit decoder using 2-bit decoders

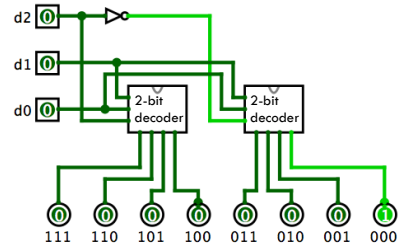

Look at decoders in simulator

Barrel shifters

Examples

The Logisim circuit examples can be found at:

<http://www.cs.pomona.edu/~dkauchak/classes/cs52/examples/logisim/>